
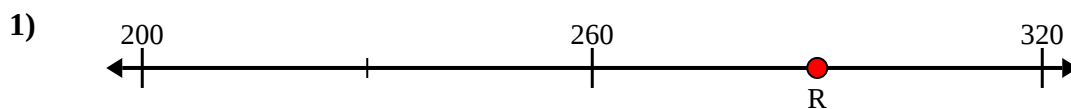


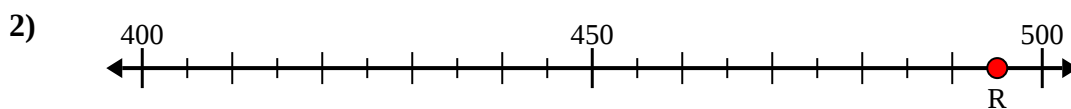


Trouvez la valeur de R

Réponses


1. _____




2. _____

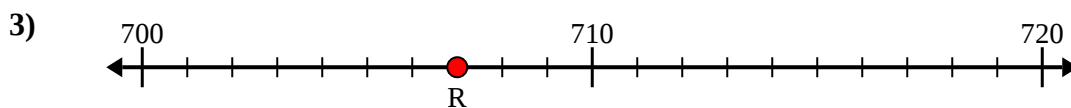


3. _____

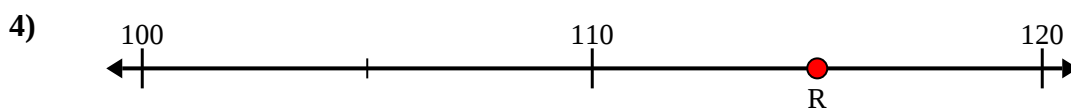


4. _____

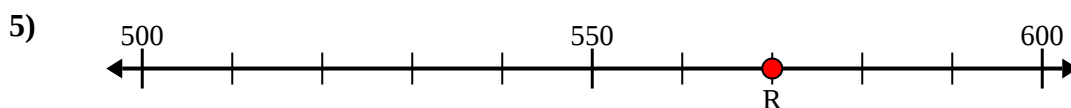


5. _____

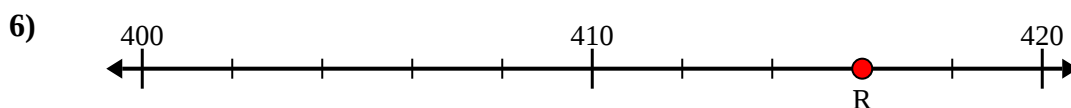


6. _____

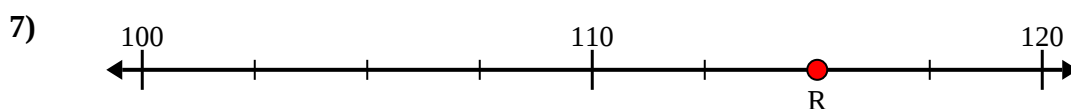


7. _____

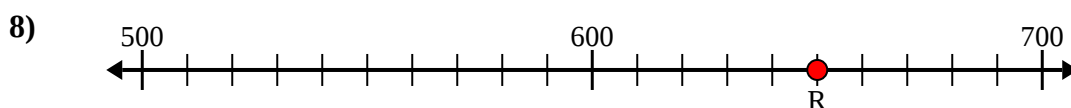

8. _____

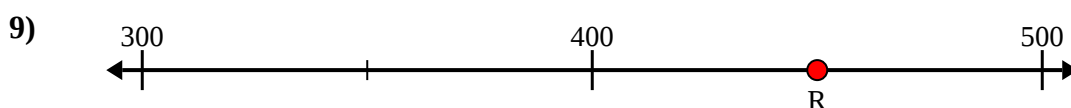











9. _____

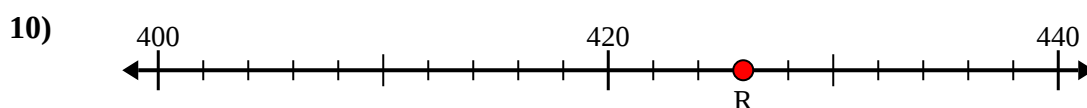

10. _____



Trouvez la valeur de R

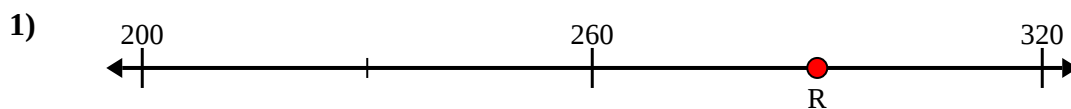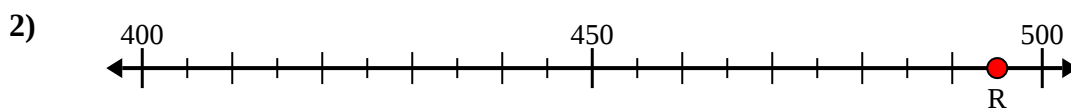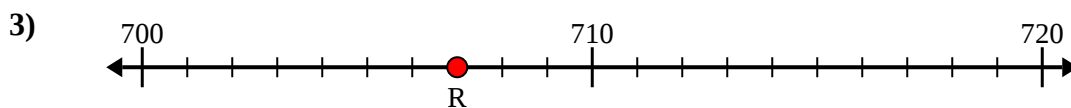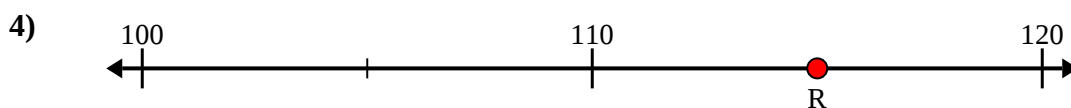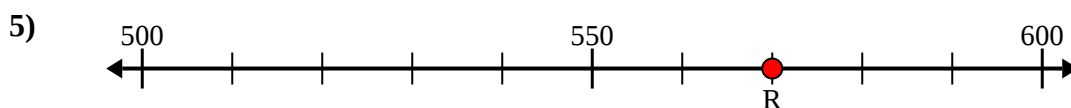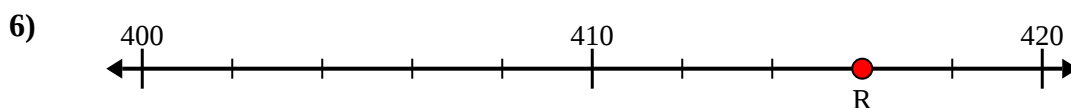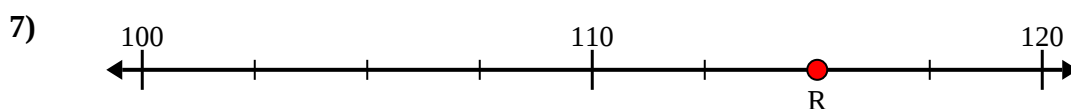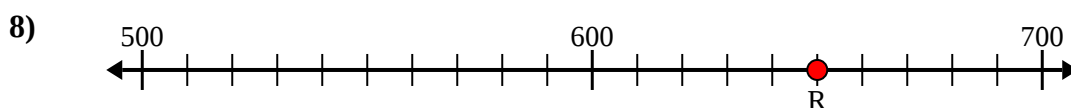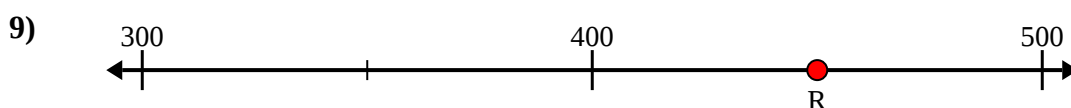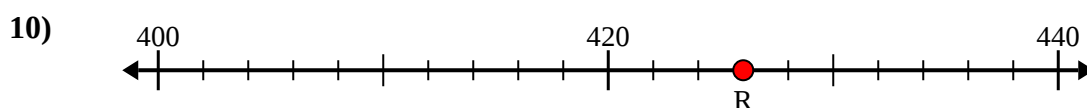Réponses1. **290**2. **495**3. **707**4. **115**5. **570**6. **416**7. **115**8. **650**9. **450**10. **426**