
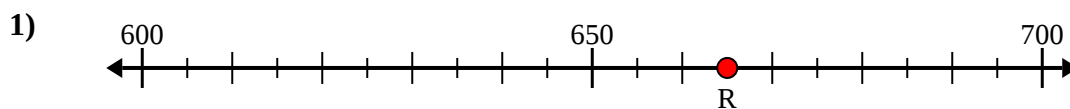


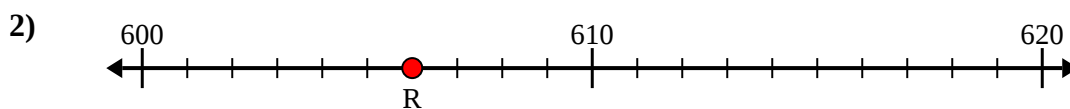


Trouvez la valeur de R

Réponses


1. _____




2. _____

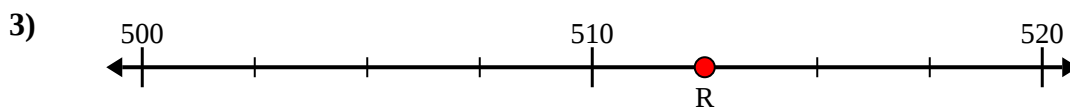


3. _____

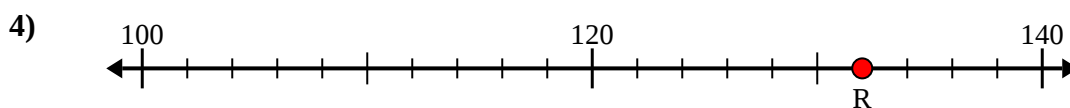


4. _____

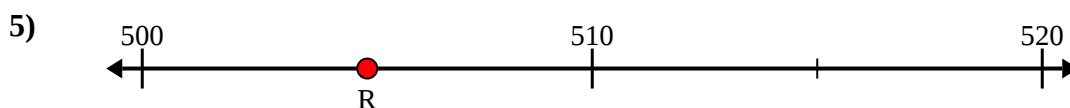


5. _____

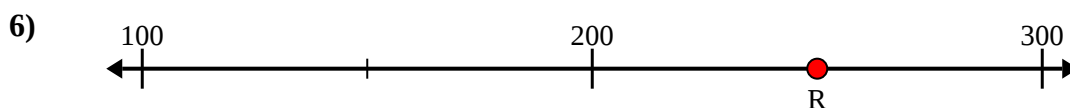


6. _____

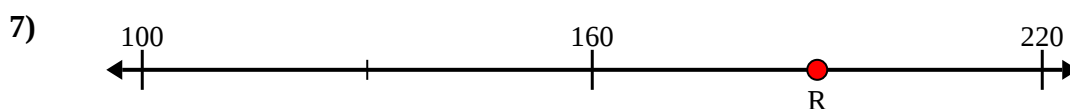


7. _____

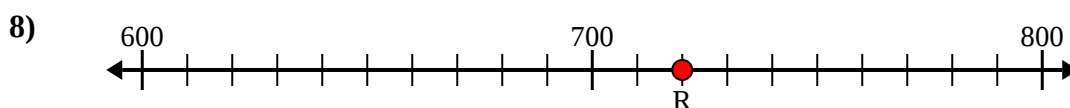

8. _____

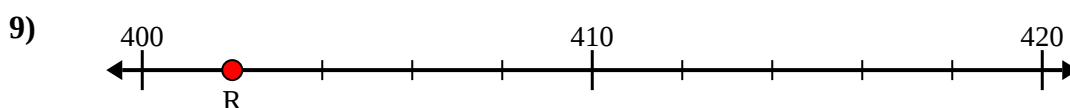











9. _____

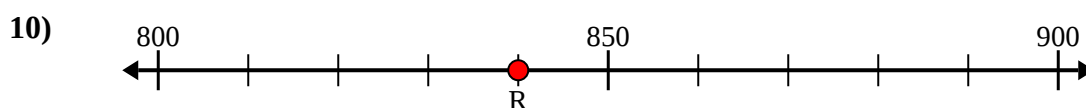

10. _____



Trouvez la valeur de R

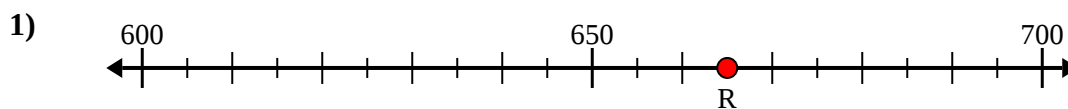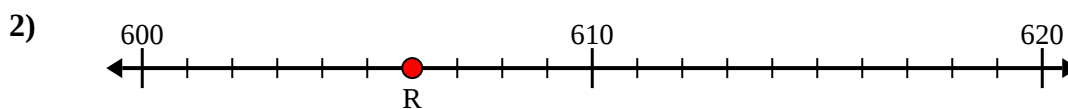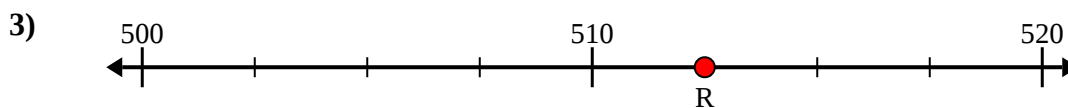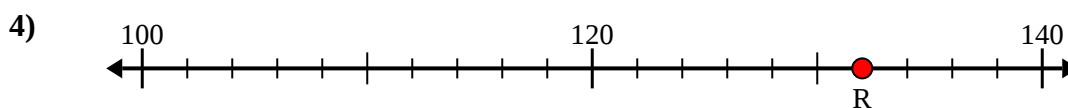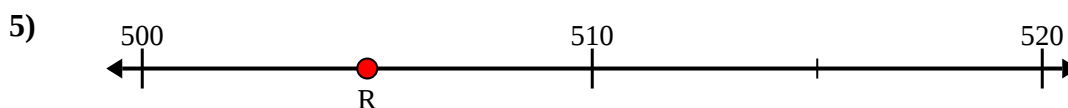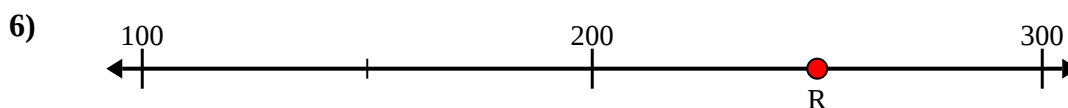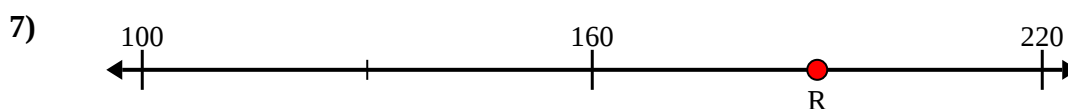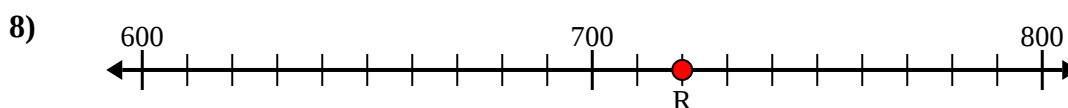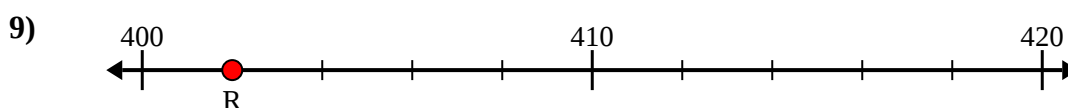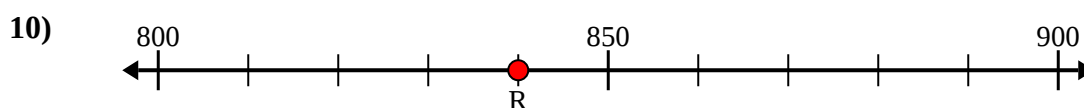Réponses1. **665**2. **606**3. **512,5**4. **132**5. **505**6. **250**7. **190**8. **720**9. **402**10. **840**