
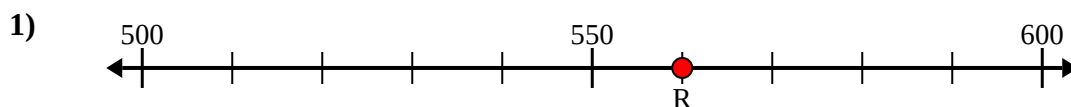


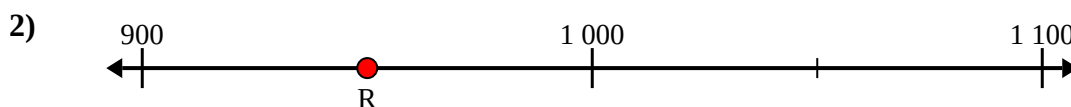


Trouvez la valeur de R

Réponses


1. _____




2. _____

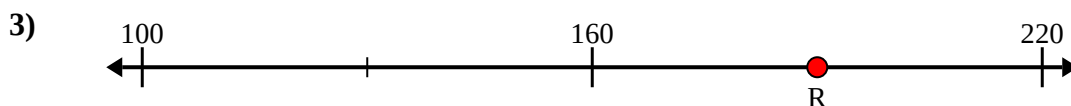


3. _____

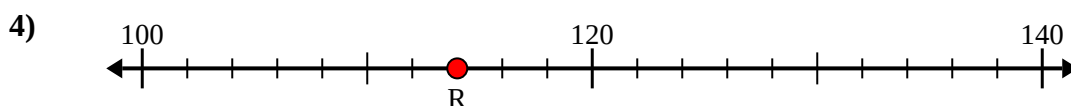


4. _____

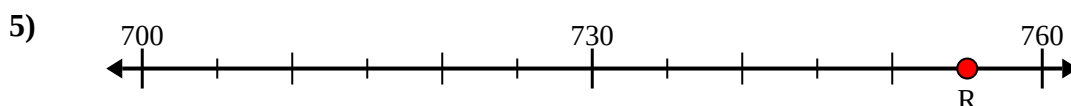


5. _____

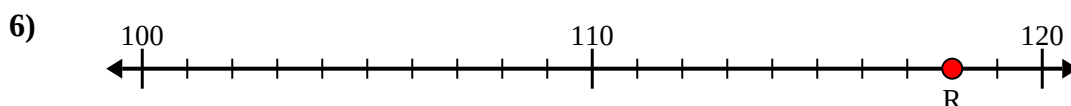


6. _____

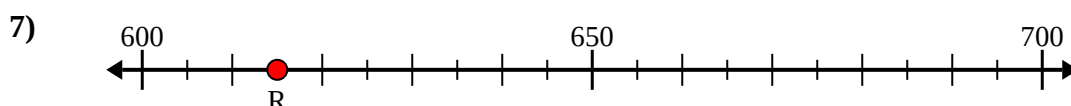


7. _____

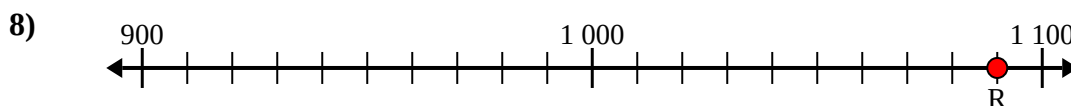

8. _____

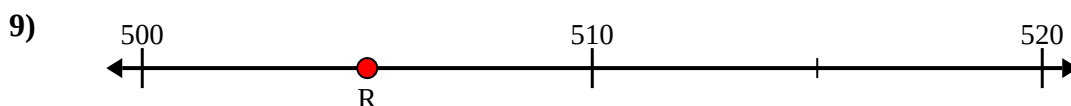











9. _____

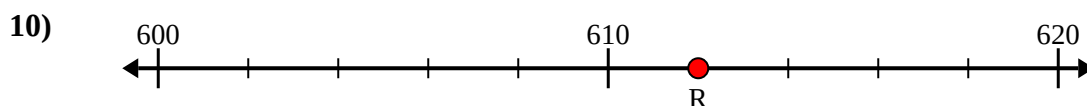

10. _____



Trouvez la valeur de R

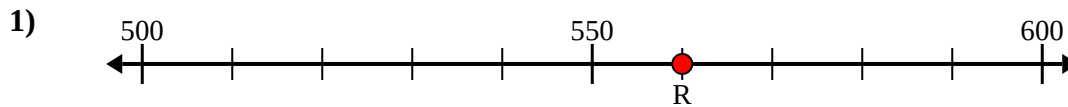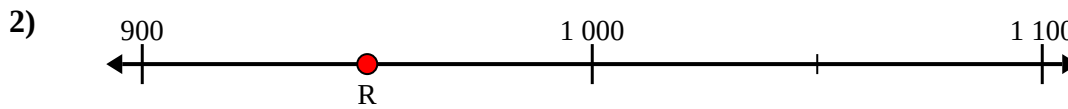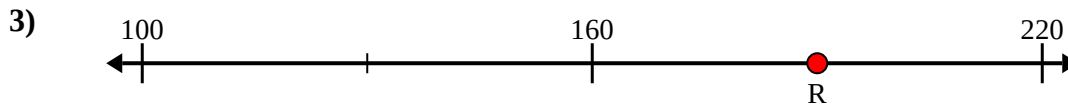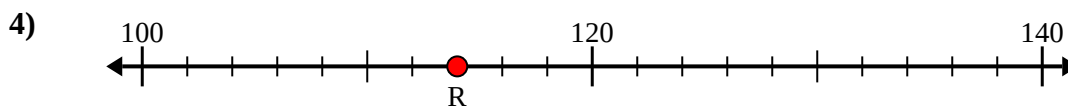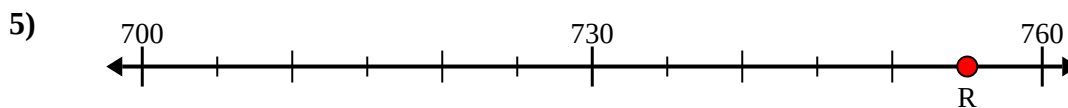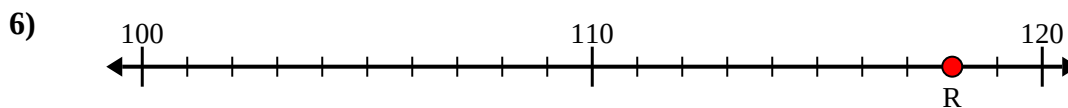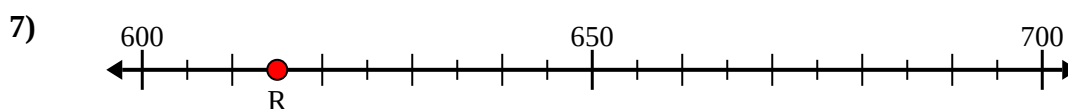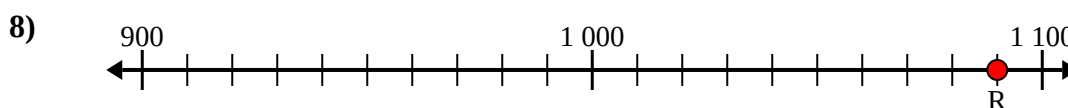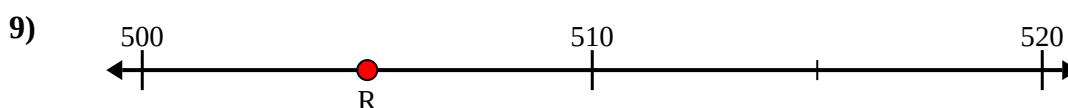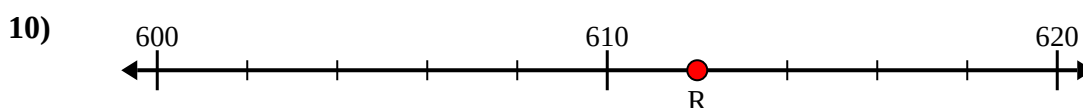Réponses1. **560**2. **950**3. **190**4. **114**5. **755**6. **118**7. **615**8. **1 090**9. **505**10. **612**